
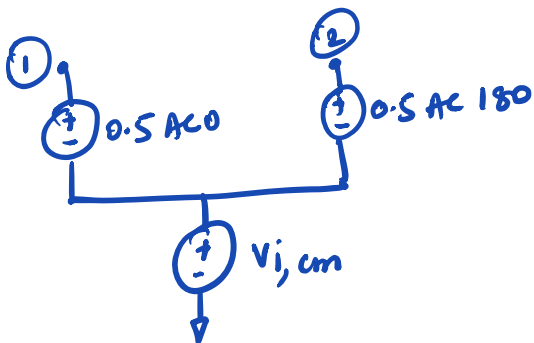


ECE 422/522 project notes:

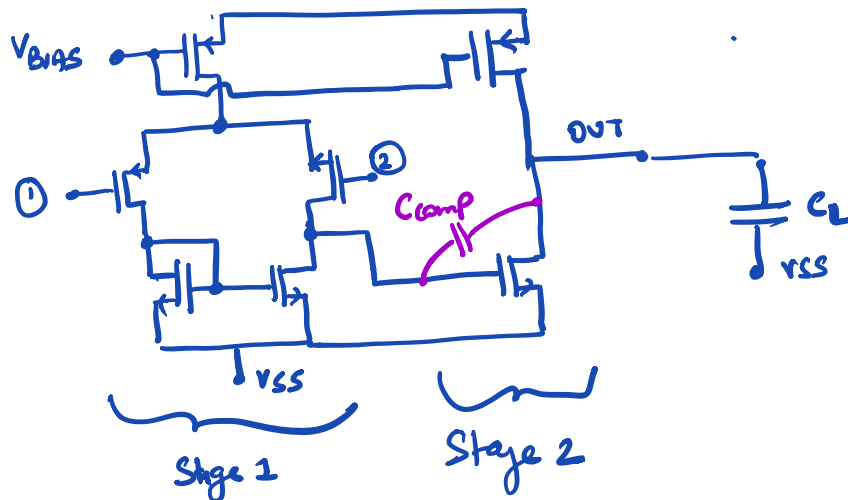1. Topology: 2 stage works well. Other topologies can also work and are welcome.



- a. generate V_{BIAS} using transistors and resistors.

- b. figure out compensation cap based on notes.

